

# A 15-Watt Direct-Coupled Amplifier

WILLIAM B. FRASER

Describing a stable, well designed amplifier suitable for high quality music reproduction or for small commercial program distribution systems.

**S**OME TIME ago the author commenced the design and construction of a high quality audio amplifier for his personal use at home. Complexity of circuit design or difficulty of adjustment were considered unimportant, for it was not intended to publish the circuit. The amplifier was finally completed and gave satisfactory results. Only then did it occur to the author that perhaps others would be interested in the design finally adopted.

The circuit is not complex, though it may appear so because of unconventional circuit arrangements. The unorthodox features include a duplex thermostatically controlled power supply, a unique form of loudness control, direct coupling throughout (except preamplifier), push-pull throughout (except preamplifier), and an input circuit permitting the use of either an unbalanced or push-pull signal. At the least, the design is an interesting study in wire. At most, in the author's opinion, it is an excellent amplifier.

Design specifications are used to define certain objectives. In this case, we wanted an amplifier that sounded as we thought it ought to sound, had no hum or tube noise, and had output power sufficient for home use. How are these requirements expressed in figures? It is difficult to say. Experts argue the problem interminably.

But there must be something more specific to aim at than the generalities just mentioned, so the following specifications were set up:

Power output: 15 watts maximum  
10 watts below 1%  
distortion from 30  
to 10,000 cps  
Frequency range: 20–20,000  $\pm$  0.5 db  
Hum and noise: inaudible at all volume levels

Gain: full output with 0.5 volts or less rms input. A preamplifier permitting the use of magnetic phonograph pickups is to be incorporated.

#### Circuit Details

The design program commenced with a study of the better known commercial circuits and a number of published diagrams. Most of these designs were more or less conventional. By great refinement, a high degree of excellence had been attained in many of them. Nevertheless, there appeared to be two general ways in which conventional design might be improved somewhat. First, almost all of these circuits employed either transformers or capacitor-resistor networks for interstage coupling, and it appeared that a part of the overall distortion of the amplifier originated in these coupling devices. Obviously, then, the elimination of coupling circuits would result in an improvement of the quality of amplification, provided the system used in lieu of conventional coupling was itself distortion free. Secondly, most of the circuits employed single-ended stages for part of the circuit rather than push-pull arrangements. It was thought that a fully push-pull circuit, if feasible, would assist in reducing the second harmonic distortion produced in most equipment.

With these preliminaries in mind, design was commenced. Low- $\mu$  triodes were tentatively decided upon for the output stage. 6A5G's were attractive, for they produced the desired power output at small distortion values: they did not require nearly as much driving voltage as the 6AS7G; they had reasonably low plate current and voltage requirements; and they were almost completely hum free.

After design and construction had been completed, it was found that the drivers were capable of providing a peak-to-peak potential of about 210 volts.

This is sufficient to drive almost any output tube. Consequently, with appropriate changes, an experimenter may substitute his favorite tube for the 6A5G's shown in the schematic. The author tried 6L6's (tetrode connected), 807's (triode connected), and 6B4G's. 6A5G's seemed to give better results than any of the others, though this is difficult to prove.

Glass enclosed triodes are used for voltage amplifiers. Both 6SN7's and 6SL7's are rugged and non-microphonic. The glass envelopes facilitate trouble shooting. In addition, glass tubes are somewhat less gassy than their metal counterparts. The use of dual triodes cuts down on the total number of tubes required and is also desirable because the two triode sections are more likely to have similar characteristics than separate tubes.

To eliminate conventional coupling devices, direct coupling is used throughout. Direct coupling is inherently free of all forms of distortion. Its principal disadvantages are the high plate supply voltage required, critical balancing, and the possibility of operating tubes at incorrect potentials. Of these problems, maintenance of balance of the circuit was found to be the most difficult to overcome. Balance was finally secured by the use of direct-coupled inverse feedback from the cathodes of the drivers. This arrangement not only corrects for tendencies of the tubes to shift their operating potentials and currents, but also maintains signal balance between the two halves of the push-pull voltage amplifier circuit.

It can be shown that plate supply resistors common to both tubes of a push-pull arrangement assist in stabilizing the d.c. potentials of a direct coupled circuit. Resistors  $R_{11}$ ,  $R_{12}$ ,  $R_{13}$ , and  $R_{14}$  have such an effect.

This feedback does not, of course, correct distortions which may arise in the output tubes and output transformer.

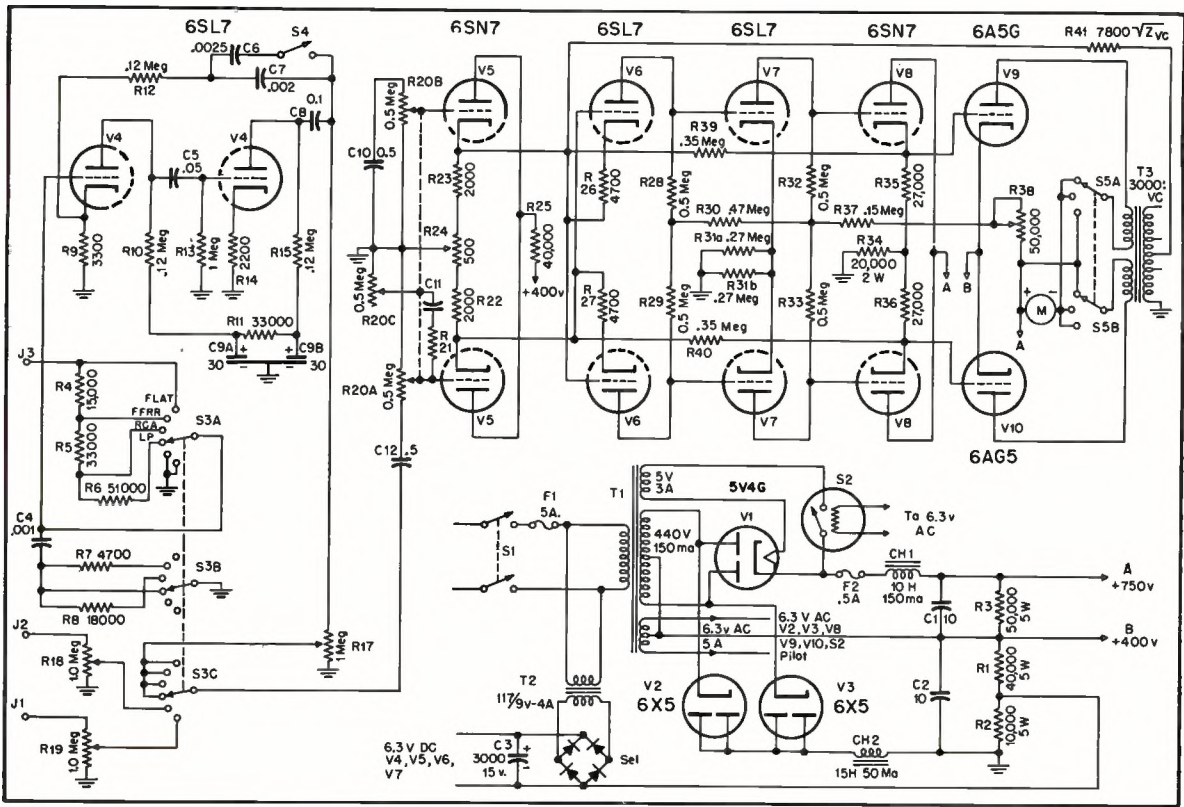


Fig. 2. Over-all schematic of the direct-coupled amplifier.

Such distortions are cancelled by inverse feedback from the output transformer secondary tap to which the loud-speaker voice coil is attached. This arrangement effectively feeds back an accurate sampling of the voltage supplied to the loud-speaker. The feedback resistor used in this circuit should have a resistance equal to 7800 times the square root of the voice coil impedance.

The values of the feedback resistors were selected after considerable investigation of the effect of feedback on signal waveform. Both sine and square wave inputs were used and the resultant oscilloscope patterns were carefully studied. Because of the small phase shift inherent in this direct-coupled circuit, unusually large amounts of feedback can be used. However, feedback in excess of that recommended will result in reduced amplification and may cause high-frequency oscillation.

Signal input can be either single ended or push-pull. Referring to Fig. 2, phase inversion is accomplished by  $V_4$  and  $V_5$  in case a single-ended signal is used. This type of phase inverter has no frequency discrimination and produces a perfectly balanced push-pull signal, provided the corresponding parts of the circuit are matched. The design was adapted from similar circuits which have been published recently. A unique form of loudness control is shown as the three-section ganged potentiometer  $R_{10}$ , capacitor  $C_{11}$  and resistor  $R_{11}$ . It will be observed that the high frequencies fed to the grid

of  $V_4$  are automatically attenuated as volume is decreased, thus giving an increased proportion of lower frequencies at reduced volume levels. The values of  $R_{11}$  and  $C_{11}$  can be varied to suit the individual. The author used a value of  $.04 \mu\text{f}$  for  $C_{11}$  and a value of 0 ohms for  $R_{11}$ . After values have been established for the elements of this loudness control, it will work with greatest effectiveness for input signals which have the same average strength as the signal for which the loudness control was originally designed. Therefore, individual semi-adjustable volume controls ( $R_{11}$ ,  $R_{15}$ ,  $R_{16}$ ) have been provided for each signal device.

In case a balanced signal is to be used instead of a single ended signal, the signal should be fed to the ungrounded ends of  $R_{20a}$  and  $R_{20b}$ .  $C_{10}$  is then attached to  $R_{20a}$  in the same way as  $C_{11}$  is attached to  $R_{11}$ . A fourth potentiometer should be ganged to the loudness control and wired similarly to  $R_{20a}$  and  $R_{20b}$ .

The slightest trace of d.c. appearing on the grid of  $V_4$  will upset the balance of the entire amplifier. Therefore,  $C_{12}$  is used to insure that d.c. from the signal sources is eliminated.

It will be noted that  $V_4$  is a cathode follower and hence produces no amplification.  $V_4$  and  $V_5$  amplify in the normal manner. The common cathode resistor of  $V_4$  tends to correct for any signal unbalance which may occur. Finally, the balanced feedback from  $V_9$  to  $V_4$  corrects

for any small residual signal unbalance. Oscilloscope tests show that the signals supplied to the output tubes are balanced under all conditions. This is an important requirement in push-pull circuits.

It will be noted that  $V_4$  has an un-bypassed cathode resistor. The resultant degeneration improves frequency response and stability.

$V_9$  is a cathode-follower driver. Since the 6A5G's are to be operated Class AB<sub>1</sub>, and presumably draw no grid current, it may be wondered why  $V_9$  is used. The principal reason for the presence of this tube is that the grids of the 6A5G's do draw current, even though they are not driven positive. This characteristic is typical of many triode-output tubes.  $V_9$  cannot supply current from its plate to the grid of the following tube without suffering serious distortion in its output. However, a cathode follower can supply the small amounts of power required without ill effects, and so this arrangement is used for the driver. An inspection of the circuit diagram will show that  $R_{10}$  controls the total plate current of the output tubes and that  $R_{11}$  balances the plate current.

A number of excellent preamplifier designs are available. The one shown has been described previously.

#### Power Supply

At first glance, the power supply may appear to be unusual. Actually, the high voltage secondary of the power trans-

former merely employs a bridge type rectifier ( $V_1, V_2, V_3$ ) so arranged that the center tap of the winding is +400 volts. This type of power supply is sometimes referred to as a "duplex" power supply.

The thermostatic delay relay is included to prevent the application of plate voltage to the output tubes before the indirectly heated cathodes of the voltage amplifiers have warmed up sufficiently to provide correct bias.

The 6.3 volt a.c. heater winding is biased at +400 volts. The cathodes of  $V_1$  and  $V_2$  are biased at +400 volts, so the same heater winding that supplies the output tubes can be used for the 6X5 heaters. Also, it will be noted that the cathode of  $V_3$  operates at approximately +327 volts which permits this same source of 6.3-volt a.c. to be used for the heater of  $V_3$ .

A full-wave selenium rectifier and associated transformer are used to provide d.c. heater current for  $V_4$  to  $V_7$ , inclusive. The use of d.c. heaters in these tubes reduces hum disturbances.

### Construction

The entire amplifier can be mounted on a 15x19 chassis, but it is recommended that the power supply be mounted on a separate chassis. If only one chassis is used, the parts must be arranged so compactly that a cooling fan is almost a necessity, especially if the amplifier is to be placed in a confined box. If a single chassis is used, the parts should be laid out so that the power supply is at the opposite end of the chassis from the low level stages. Since the circuit is completely push-pull (except for the preamplifier), hum is minimized and shielded wire need not be used. However, the preamplifier must be carefully shielded.

The use of a single ground and grounding bus is recommended to avoid hum which sometimes results from multiple grounds. In this case of the preamplifier, an insulated input jack should be used. The grounded side of this jack should be attached to the grounded end of  $R_1$ . If this precaution is not observed, a high hum level will almost invariably result.

In the interest of good construction, filter capacitors  $C_1$  and  $C_2$  should be oil filled. Because of the push-pull arrangement with its inherent hum cancellation characteristics, no large capacitance electrolytic capacitors are required except in the case of the preamplifier and d.c. heater supply.

It is not absolutely essential to match resistors, capacitors, tubes, etc., of the two halves of the push-pull circuit, because cross-coupling, cathode degeneration, inverse feedback, and balancing potentiometers provide for a reasonably well balanced output, even if exact push-pull symmetry is not maintained. Nevertheless, accurate balance and superior performance of the amplifier can be attained only by electrical and mechanical symmetry. Furthermore, changing line voltage will result in unbalanced opera-

tion if parts are not fairly carefully matched. Therefore, matching of corresponding parts is recommended insofar as possible.

Wiring of those portions of the circuit operating at +400 volts or less should follow conventional procedure. For the higher voltages, wire with fibre glass insulation is recommended.

Potentiometers  $R_{11}$  and  $R_{12}$  should be so located that they can be reached easily with a screwdriver while the amplifier is in operation.

Transformers and chokes should be of good quality. The output transformer is especially important. The quality of the entire amplifier will depend largely on this item. This circuit was designed, among other things, to eliminate expensive interstage audio transformers, and the money so saved can be invested in the output transformer. A number of excellent makes are available. The author used a UTC linear standard LS55, and found it very satisfactory.

Tubes  $V_4$ ,  $V_5$ , and  $V_6$  should be

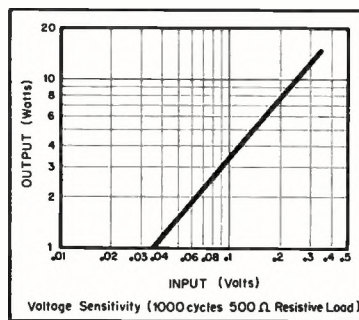


Fig. 3. Curve showing voltage sensitivity of the amplifier when feeding a 500-ohm resistive load.

mounted in non-microphonic tube sockets. Switches  $S_1$  and  $S_2$  should be the shorting type to prevent noisy switching. The feedback loop attached to the secondary of the output transformer should not be finally soldered in place until adjustments of the amplifier are completed.

### Adjustment

After completing the construction, insert all tubes heated by d.c. Turn on the amplifier and check the heater voltage to make sure it is 6.0 to 6.3 volts.

Next, insert all tubes heated by a.c. The thermostatic switch should not be inserted until later. Turn on set and measure a.c. heater voltage.

If everything is operating normally, place the thermostatic switch in its socket and turn on the amplifier. Adjust  $R_{11}$  and  $R_{12}$  to produce correct operating current and voltages for the output tubes. If parts have been well balanced, minimum hum will be obtained when plate currents are balanced. If parts have not been carefully selected, minimum hum may occur when plate currents are slightly unbalanced. Adjust  $R_{11}$  for minimum hum.

Finally, attach feedback loop from

output transformer secondary to one of the cathodes of  $V_1$ . If noise increases when feedback loop is attached, the loop has been reversed and should be attached to the other cathode.

A final check of voltages should be made; Table I shows typical values for plate, grid, and cathode potentials referred to ground. If everything is in correct working order, hum and noise will be inaudible when the ear is held more than three or four inches from the speaker. When the preamplifier is switched into the circuit, a small amount of noise will become apparent, though this noise should be so slight as to cause no objection.

In order to maintain balance of the amplifier, potentiometers  $R_{11}$  and  $R_{12}$  will have to be adjusted periodically as the tubes age. The frequency of these adjustments will decrease after the first few weeks of operation, during which time the tubes' characteristics are changing quite rapidly. Since line voltages will vary throughout the day, it is suggested that balancing be done when the line voltage is at its average value. The amplifier should be adjusted only after it has warmed up at least half an hour.

### Performance

Full output of 15 watts is attained with an input voltage of 0.35 volts rms. An output of over 20 watts can be attained, though the amplifier begins to produce appreciable distortion over 15 watts.

Frequency response is flat to approximately 20,000 cps, with a gradual droop above that point. Voltage sensitivity is shown in Fig 3. Hum and noise voltages were so low that they could not be measured with equipment available.

### Conclusions

In the past, direct-coupled amplifiers have proved unpopular probably because of several problems associated with this type of design. The circuit described herein overcomes all these difficulties by unconventional arrangements, except that periodic adjustment of the current of output tubes will be required.

However, for those who require unusually good performance, and enjoy the work of achieving it, it is believed that this circuit will provide satisfactory results. Its superiority to most typical designs can be shown either by instruments or by listener tests.

TABLE I

Tube	Plate	Grid	Cathode
V5	170	0	6.5
V6	120	6.5	8
V7	309	120	122.7
V8	750	309	327
V9	745 @ 42 ma	327	400
V10	745 @ 42 ma	327	400

NOTE 1. Actual voltages may vary as much as 15 per cent from figures shown without detrimental effect. However, output tube plate current and voltage should be adjusted as accurately as possible. The exact voltage of output tube grids is unimportant, provided plate current and voltage are correct.

NOTE 2. Voltage measurements should be made with a vacuum tube voltmeter.

## PARTS LIST

R <sub>1</sub>	40,000 ohms, 5-watt, wire wound	R <sub>26</sub> , R <sub>27</sub>	4700 ohms, 1-watt	V <sub>4</sub> , V <sub>6</sub> , V <sub>7</sub>	6SL7
R <sub>2</sub>	10,000 ohms, 5-watt, wire wound	R <sub>28</sub> , R <sub>29</sub> , R <sub>32</sub>	0.5 meg. 1-watt	V <sub>8</sub> , V <sub>9</sub>	6SN7
R <sub>3</sub>	50,000 ohms, 5-watt, wire wound	R <sub>30</sub>	0.47 meg. 1-watt	V <sub>9</sub> , V <sub>10</sub>	6A5G
R <sub>4</sub>	15,000 ohms, 1/2-watt	R <sub>31</sub>	0.135 meg (2 0.27-meg 1-watt resistors in parallel)	S <sub>1</sub>	DPST toggle switch
R <sub>5</sub>	33,000 ohms, 1/2-watt	R <sub>34</sub>	20,000 ohms, 2-watt	S <sub>2</sub>	Amperite 20-sec delay relay
R <sub>6</sub>	51,000 ohms, 1/2-watt	R <sub>35</sub> , R <sub>38</sub>	27,000 ohms, 2-watt	S <sub>3</sub>	3-gang, 6-position, shorting type
R <sub>7</sub>	4700 ohms, 1/2-watt	R <sub>37</sub>	0.15 meg, 1-watt	S <sub>4</sub>	SPST toggle switch
R <sub>8</sub>	18,000 ohms, 1/2-watt	R <sub>38</sub>	50,000-ohm wirewound potentiometer	S <sub>5</sub>	2-gang, 3-position, shorting type
R <sub>9</sub>	3300 ohms, 1/2-watt	R <sub>39</sub> , R <sub>10</sub>	0.35 meg. 2-watt	T <sub>1</sub>	440-0-440v at 150 ma; 5v at 3a; 6.3v at 5a
R <sub>10</sub> , R <sub>18</sub>	0.12 meg. 1-watt	R <sub>41</sub>	7800 $\sqrt{V.C.}$ impedance	T <sub>2</sub>	9v at 4a filament transformer
R <sub>11</sub>	33,000 ohms, 1-watt	C <sub>1</sub> , C <sub>2</sub>	10 $\mu$ f, 600-volt, oil filled	T <sub>3</sub>	20-watt output transformer, 3000 ohms plate-to-plate
R <sub>12</sub>	0.12 meg, 1/2-watt	C <sub>3</sub>	3000 $\mu$ f, 15-volt electrolytic	F <sub>1</sub>	5-amp fuse
R <sub>13</sub>	1.0 meg. 1/2-watt	C <sub>4</sub>	.001 $\mu$ f, mica	F <sub>2</sub>	0.5-amp fuse
R <sub>14</sub>	2200 ohms, 1/2-watt	C <sub>5</sub>	.05 $\mu$ f, 600-volt, tubular	SEL	15-volt. 4-amp selenium rectifier
R <sub>15</sub>	75,000 ohms, 1-watt (Not shown, but connects C <sub>30</sub> to 400-volt supply at "B")	C <sub>6</sub>	.0025 $\mu$ f, mica	M	Milliammeter, 0-100 ma
R <sub>17</sub> , R <sub>18</sub> , R <sub>19</sub>	1-meg potentiometer	C <sub>7</sub>	.002 $\mu$ f, mica	Ch <sub>1</sub>	10-henry, 150-ma choke
R <sub>20</sub>	3-sect. ganged potentiometer. 0.5 meg. each section	C <sub>8</sub>	0.1 $\mu$ f, 600-volt, tubular	Ch <sub>2</sub>	15-henry, 50-ma choke
R <sub>21</sub>	See text	C <sub>9</sub>	30-30 $\mu$ f, 450-volt, electrolytic	J <sub>1</sub> , J <sub>2</sub> , J <sub>3</sub>	Input jacks
R <sub>22</sub> , R <sub>23</sub>	2000 ohms, 1-watt	C <sub>10</sub> , C <sub>12</sub>	0.5 $\mu$ f, 600-volt, oil filled		
R <sub>24</sub>	500-ohm wire-wound potentiometer	C <sub>11</sub>	See text		
R <sub>25</sub>	40,000 ohms, 10-watt, wire wound	V <sub>1</sub>	5V4G		
		V <sub>2</sub> , V <sub>3</sub>	6X5		