

The high end of a newly installed system may sound sweet and smooth, until you find out it's been rolled off by an interaction between component and cable.

Herman Burstein

Every serious audiophile should be alert to possible treble loss caused by a component's high output impedance or the high capacitance of his interconnect cable. If we let R stand for output impedance in ohms, and let C stand for cable capacitance in μF (microfarads), and then multiply one by the other, the result, RC , will show if there is significant treble loss; we want low RC .

What is *significant* treble loss? Of course, it varies with hearing ability, taste, and quite possibly other factors. But as a rough guide we may think of *good* high-end frequency response as being down by no more than 3 dB at 20 kHz (except for FM, which is limited to 15 kHz). *Excellent* response would be no more than 1 dB down, and *purist* no more than 0.25 dB down.

Output impedance, which is essentially resistive and therefore called R , is independent of frequency. But capacitive impedance, labelled X_C , declines as frequency rises. Output impedance R and capacitive impedance X_C form a voltage divider across the signal, with the voltage portion across X_C going to the next component in the chain. As frequency rises, X_C declines relative to R so that the voltage across X_C drops, causing treble loss. Thus, at a given frequency, loss is determined by the ratio of R divided by X_C ; the smaller this ratio, the smaller the loss. Because X_C varies inversely with cable capacitance C , we may substitute C for 1 divided by X_C and therefore say that the smaller RC is, the smaller the loss will be at a given frequency.

As can be seen in Table I, treble loss is insignificant when RC is 1 or less. Fortunately, the output impedance of tape decks, preamps, CD players, surround sound processors, equalizers, etc., tends to be quite low today, usually under 1 kilohm. (The output impedance of even fairly long interconnects is usually below 0.001 μF .) The resulting RC is usually below 1, and treble

Impedance, Cables & Treble Loss

response is safe. On the other hand, some components have output impedances of several thousand ohms—as high as 10 kilohms in the case of one passive preamp—and some audiophiles employ unusual or very long cables.

As a "good" scenario, assume a CD player has an output impedance of 200 ohms—quite typical—and that its interconnect to the preamp is a 6-foot, heavy-duty cable whose capacitance

is 30 pF (picofarads) per foot. (One picofarad is one-millionth of 1 μ F, so to convert pF to μ F, we divide pF by 1,000,000.) Accordingly, the cable's capacitance is 180 pF, or 0.00018 μ F. Therefore

$$RC = 200 \times 0.00018 = 0.036.$$

Treble response is safe indeed!

Now, for the opposite scenario. In an actual case, a CD player's output im-

pedance was found to vary with the setting of its output control; it measured as high as 4,475 ohms. Assume that this CD player is fed directly to the power amplifier, located close to the speakers and requiring a 30-foot interconnect (big listening room). Assume further that the cable's capacitance is 50 pF per foot, for a total of 1,500 pF—or 0.0015 μ F. (Although conventional shielded cable of high quality typically has capacitance of 25 to 30 pF per foot, the capacitance of some cables, including exotic ones, may be appreciably higher, perhaps as high as 70 pF per foot. Hence 50 pF per foot is not an unreasonable assumption for a bad-case scenario.) In this example, RC could be as great as 6.7125 (the product of 4,475 and 0.0015). As Table I reveals, RC this high produces a loss greater than 2 dB at 20 kHz.

Table I shows loss, in dB, at 10, 15, 20, and 25 kHz for RC values from 1 to 10. To illustrate, if RC is 3, the respective losses at 10, 15, 20, and 25 kHz are 0.152, 0.334, 0.577, and 0.871 dB. (The dB values in the Table have been rounded off.) An RC of 6.7125, as in our example above, produces a loss between 1.96 dB and 2.49 dB at 20 kHz; from the formula at the bottom of the Table, we find the exact loss to be 2.33 dB. At 10 kHz, the loss is 0.71 dB; and at 15 kHz, 1.46 dB, while at 25 kHz, it is 3.25 dB.

While a loss such as 2.33 dB at 20 kHz may not seem distressing, it must be recognized that RC losses are additive. If more than two electronic components are in the audio chain, individual RC losses that are not serious in and of themselves may add up to a total that is significant. (Moreover, there can be treble losses *within* components to be taken into account, possibly adding something on the order of a 1- to 3-dB loss at 20 kHz.)

Summing up, it appears wise to mind not only your Ps and Qs, but also your Rs and Cs. ▲

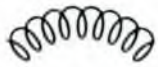


Table I—Treble loss at selected frequencies for selected RC values.

RC	Loss, dB			
	At 10 kHz	At 15 kHz	At 20 kHz	At 25 kHz
1	0.02	0.04	0.07	0.11
2	0.07	0.15	0.27	0.41
3	0.15	0.33	0.58	0.87
4	0.27	0.58	0.98	1.45
5	0.41	0.87	1.45	2.09
6	0.58	1.21	1.96	2.76
7	0.77	1.57	2.49	3.44
8	0.98	1.96	3.03	4.12
9	1.21	2.35	3.58	4.77
10	1.45	2.76	4.12	5.40

Loss is calculated by using the formula:

$$L = 20 \log \sqrt{1 + (JRC)^2}$$

where L is the loss in dB at frequency f, R is the output impedance in ohms, C is the cable capacitance in μ F, and J is f divided by 159,155.

To find the RC value corresponding to a given loss L at a given frequency f:

$$RC = K \sqrt{10^{0.1L} - 1}$$

where K is 159,155 divided by f.

